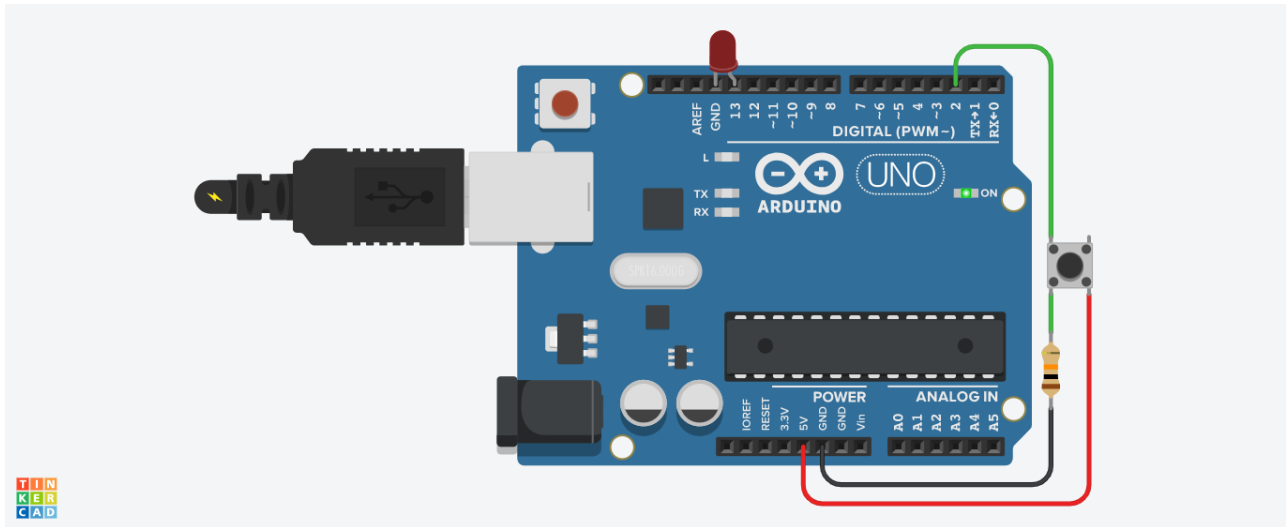


## Experiment

# Design a Door Bell With Button.

### Circuit diagram:



## Theory:

### CONCEPT USED:

- By using kirchoff's voltage law
- &
- By using kirchoff's current law
- Series or parallel connections

## LEARNING AND OBSERVATIONS:

- **Connections in Breadboard and wiring.**
- **How to control arduino and its coding.**
- **Use of multimeter for continuity.**

## **OBSERVATION:**

- Blinking of leds in a pattern and in chasing form.
- Relation between software and hardware.

## **PROBLEMS & TROUBLESHOOTING:**

- To select the right port and type of arduino
- To check the loose connections
- To check the connections according to the codes
- To check the continuity of the circuit
- To check the flow of current in the circuit

## **PRECAUTIONS:**

- Handle tools carefully
- Wear gloves
- Do not connect arduino till the circuit is complete

## **OUTCOMES:**

- LEDs glows in a chasing pattern
- It can be used as for decorating purpose

**Created By-**

Name: SARVEKASH AGGARWAL

ROLLNO: 19BCS4519

Stream: CSE(IOT 1A)

University: CHANDIGARH UNIVERSITY